
RISC-V Processor Design

Daniel Chen Berkeley EECS 251 LA

5-Stage Pipeline: IF/ ID/ EX/ MEM/ WB

 

Control Unit


- Input:
 - Opcode
 - funct3 (1-bit)
 - CSRRW: **0**01
 - CSRRWI: **1**01
- Output:
 - Asel, Bsel
 - PC or data from register
 - if_rs1, if_rs2
 - Forwarding unit

```
`OPC ARI RTYPE:
begin
   if_rs1 = 1'd1;
   if_rs2 = 1'd1;
   btype = 1'd0;
   jtype = 1'd0;
   stype = 1'd0;
   csrtype = 1'd0;
   RegWEn = 1'd1; //write to reg
   Asel = 1'd0; //not deal with hazard
   Bsel = 1'd0; //not deal with hazard
   memRW = 1'd0; //not write
   memtoreg = 2'd1; //choose alu_out
   //don't care
   dataW_sel = 2'd0;
end
```

Forwarding Unit

- Generate A_sel/ B_sel
- For B-type:

Using ALU to calculate PC_nxt

 

Branch Predictor (ID-stage)


# of cycles	w/o BrPred	2-bit	1-bit	Always Taken
cachetest	90410	90409	90410	88368
final	6415	6408	6415	6264
fib	5558	5558	5558	5412
sum	76102	76037	76102	73961
replace	76176	76109	76176	74038

Tested on test_bmark_short

Cache (Write Back + Allocate on miss)

Direct-Mapped

 
- Data: 4 x SRAM1RW 256x128 (32 entries used)
- Dirty/Valid/Tag:
 - Implemented with regs



Cache (Write Back + Allocate on miss)


2-Way Associative

 - Data: 8x **SRAM1RW 256x128 (32 entries used)**
- Replacement:
 - Least Recently Used policy
- LRU/Dirty/Valid/Tag:
 - Implemented with regs



Read Only Cache

 - For I\$
- INIT state:
 - SRAM didn't initialize



Cache with **Write Buffer** State != Read Mem or ~mem reg rdy or ~mem_resp_ready_but_dirty Memory Interface: Write State == Read Mem and mem_req_rdy and mem resp_ready_but_dirty if (state == Before read): Before Write IDLE Update write Buffer mem req rdy mem req rdy mem reg data rdy and wb cnt != 3'd3 mem reg rdy and mem resp valid Cache Interface: if(hit): write cpu index, dirty ~miss Cache Interface: Write in Cache Write mem resp data **CPU Interface:** Stall ~mem_req_data_rdy Write Back Before Idle mem_req_data_rdy Cache Interface: Read Update valid, tag, dirty. cpu req write and wb_cnt == 3'd3 **CPU Interface: Stall** if(miss): follow cpu index MEM Interface: Read && cpu rdy else follow cpu reg addr Memory Interface: Write Write **IDLE CPU Interface:** ~mem resp valid if(miss): Stall hit wb state else Dont Stall miss ~hit mem reg rdy and mem resp valid Cache Interface: Write in Cache Write mem resp data Before Read mem_req_rdy Read Mem ~mem reg rdy Update valid, tag, dirty... wb state == IDLE **CPU Interface:** Stall MEM Interface: Read Memory Interface: Read from mem CPU Interface: Stall ~mem resp valid **Read and Write**

Functionality (test_asm/ test_bmark)

```
/home/cc/eecs151/fl21/class/eecs151-abv/scratch/eecs151-abv/project/asm output/addi.out
                                                                                                       () after 381 simulation cycles
PASSED
         /home/cc/eecs151/fl21/class/eecs151-aby/scratch/eecs151-aby/project/asm_output/add.out
                                                                                                         after 689 simulation cycles
PASSED
         /home/cc/eecs151/fl21/class/eecs151-aby/scratch/eecs151-aby/project/asm_output/andi.out
                                                                                                       () after 321 simulation cycles
                                                                                                       () after 707 simulation cycles
PASSED
         /home/cc/eecs151/fl21/class/eecs151-abv/scratch/eecs151-abv/project/asm_output/and.out
PASSED
         /home/cc/eecs151/fl21/class/eecs151-abv/scratch/eecs151-abv/project/asm_output/auipc.out
                                                                                                       () after 130 simulation cycles
PASSED
         /home/cc/eecs151/fl21/class/eecs151-abv/scratch/eecs151-abv/project/asm_output/beg.out
                                                                                                         after 496 simulation cycles
PASSED
         /home/cc/eecs151/fl21/class/eecs151-abv/scratch/eecs151-abv/project/asm_output/bge.out
                                                                                                          after 535 simulation cycles
PASSED
         /home/cc/eecs151/fl21/class/eecs151-abv/scratch/eecs151-abv/project/asm_output/bgeu.out
                                                                                                         after 550 simulation cycles
PASSED
         /home/cc/eecs151/fl21/class/eecs151-abv/scratch/eecs151-abv/project/asm_output/blt.out
                                                                                                         after 495 simulation cycles
PASSED
         /home/cc/eecs151/fl21/class/eecs151-aby/scratch/eecs151-aby/project/asm_output/bltu.out
                                                                                                         after 508 simulation cycles
PASSED
                                                                                                         after 492 simulation cycles
         /home/cc/eecs151/fl21/class/eecs151-abv/scratch/eecs151-abv/project/asm output/bne.out
PASSED
         /home/cc/eecs151/fl21/class/eecs151-aby/scratch/eecs151-aby/project/asm_output/ial.out
                                                                                                          after 127 simulation cycles
PASSED
         /home/cc/eecs151/fl21/class/eecs151-aby/scratch/eecs151-aby/project/asm_output/jalr.out
                                                                                                         after 227 simulation cycles
PASSED
         /home/cc/eecs151/fl21/class/eecs151-abv/scratch/eecs151-abv/project/asm_output/lb.out
                                                                                                         after 386 simulation cycles
PASSED
                                                                                                         after 386 simulation cycles
         /home/cc/eecs151/fl21/class/eecs151-abv/scratch/eecs151-abv/project/asm_output/lbu.out
PASSED
         /home/cc/eecs151/fl21/class/eecs151-abv/scratch/eecs151-abv/project/asm_output/lh.out
                                                                                                         after 414 simulation cycles
PASSED
         /home/cc/eecs151/fl21/class/eecs151-abv/scratch/eecs151-abv/project/asm output/lhu.out
                                                                                                          after 415 simulation cycles
PASSED
         /home/cc/eecs151/fl21/class/eecs151-aby/scratch/eecs151-aby/project/asm_output/lui.out
                                                                                                         after 139 simulation cycles
PASSED
         /home/cc/eecs151/fl21/class/eecs151-abv/scratch/eecs151-abv/project/asm_output/lw.out
                                                                                                         after 410 simulation cycles
PASSED
         /home/cc/eecs151/fl21/class/eecs151-abv/scratch/eecs151-abv/project/asm output/ori.out
                                                                                                         after 331 simulation cycles
PASSED
         /home/cc/eecs151/fl21/class/eecs151-aby/scratch/eecs151-aby/project/asm output/or.out
                                                                                                         after 704 simulation cycles
                                                                                                         after 651 simulation cycles
PASSED
         /home/cc/eecs151/fl21/class/eecs151-abv/scratch/eecs151-abv/project/asm_output/sb.out
PASSED
                                                                                                         after 732 simulation cycles
         /home/cc/eecs151/fl21/class/eecs151-aby/scratch/eecs151-aby/project/asm_output/sh.out
PASSED
         /home/cc/eecs151/fl21/class/eecs151-abv/scratch/eecs151-abv/project/asm output/simple.out
                                                                                                         after 100 simulation cycles
PASSED
         /home/cc/eecs151/fl21/class/eecs151-aby/scratch/eecs151-aby/project/asm_output/slli.out
                                                                                                         after 387 simulation cycles
PASSED
         /home/cc/eecs151/fl21/class/eecs151-abv/scratch/eecs151-abv/project/asm_output/sll.out
                                                                                                         after 734 simulation cycles
PASSED
         /home/cc/eecs151/fl21/class/eecs151-abv/scratch/eecs151-abv/project/asm_output/slti.out
                                                                                                         after 381 simulation cycles
PASSED
         /home/cc/eecs151/fl21/class/eecs151-abv/scratch/eecs151-abv/project/asm_output/sltiu.out
                                                                                                         after 379 simulation cycles
PASSED
         /home/cc/eecs151/fl21/class/eecs151-abv/scratch/eecs151-abv/project/asm_output/slt.out
                                                                                                       () after 683 simulation cycles
PASSED
         /home/cc/eecs151/fl21/class/eecs151-abv/scratch/eecs151-abv/project/asm_output/sltu.out
                                                                                                         after 683 simulation cycles
PASSED
         /home/cc/eecs151/fl21/class/eecs151-abv/scratch/eecs151-abv/project/asm_output/srai.out
                                                                                                         after 402 simulation cycles
PASSED
         /home/cc/eecs151/fl21/class/eecs151-abv/scratch/eecs151-abv/project/asm_output/sra.out
                                                                                                         after 755 simulation cycles
PASSED
         /home/cc/eecs151/fl21/class/eecs151-aby/scratch/eecs151-aby/project/asm_output/srli.out
                                                                                                         after 396 simulation cycles
PASSED
         /home/cc/eecs151/fl21/class/eecs151-abv/scratch/eecs151-abv/project/asm output/srl.out
                                                                                                       () after 744 simulation cycles
PASSED
         /home/cc/eecs151/fl21/class/eecs151-aby/scratch/eecs151-aby/project/asm_output/sub.out
                                                                                                         after 678 simulation cycles
PASSED
                                                                                                       () after 730 simulation cycles
         /home/cc/eecs151/fl21/class/eecs151-abv/scratch/eecs151-abv/project/asm_output/sw.out
PASSED
         /home/cc/eecs151/fl21/class/eecs151-abv/scratch/eecs151-abv/project/asm_output/xori.out
                                                                                                       () after 333 simulation cycles
PASSED 1
                                                                                                       () after 707 simulation cycles
         /home/cc/eecs151/fl21/class/eecs151-abv/scratch/eecs151-abv/project/asm_output/xor.out
        /home/cc/eecs151/fl21/class/eecs151-abv/scratch/eecs151-abv/project/bmark output/cachetest.out
                                                                                                    () after 3016974 simulation cycles
        /home/cc/eecs151/fl21/class/eecs151-abv/scratch/eecs151-abv/project/bmark_output/final.out
                                                                                                   () after 6264 simulation cycles
        /home/cc/eecs151/fl21/class/eecs151-abv/scratch/eecs151-abv/project/bmark_output/fib.out () after 5412 simulation cycles
        /home/cc/eecs151/fl21/class/eecs151-abv/scratch/eecs151-abv/project/bmark_output/sum.out () after 19091565 simulation cycles
       /home/cc/eecs151/fl21/class/eecs151-abv/scratch/eecs151-abv/project/bmark_output/replace.out
                                                                                                   () after 19559246 simulation cycles
```


Runtime Analysis

(2-way associative + always taken)

Test Cases	# of cycles	Clock period (ns)	Runtime (s)
cachetest	3016974	1.3	3.922* 10 ⁻³
final	6264	1.3	8.143* 10 ⁻⁶
fib	5412	1.3	7.036* 10 ⁻⁶
sum	19091565	1.3	2.482* 10 ⁻²
replace	19559246	1.3	2.542* 10 ⁻²

Floorplan

 - Floorplan dimension:
 - Width x Height = 700×800
 - Area = $560,000 \text{ um}^2$
- Area utilization (density):
 - Riscv_top: 197711 um^2
 - 197711 / 560000 = 35%



Power (Innovus Estimated)


- Static power estimation (activity factor = 0.2)


Total Power		
Total Internal Power:	4.78074122	26.0319%
Total Switching Power:	11.55955628	62.9437%
Total Leakage Power:	2.02461838	11.0244%
Total Power:	18.36491586	

Group	Internal Power	Switching Power	Leakage Power	Total Power	Percentage (%)
Sequential	2.594	0.1136	0.5464	3.254	17.72
Macro	0	0.1515	0	0.1515	0.8247
10	0	0	5.536e-07	5.536e-07	3.014e-06
Combinational	1.94	10.69	1.448	14.08	76.68
Clock (Combinational)	0.09363	0.3244	0.0001642	0.4182	2.277
Clock (Sequential)	0.1527	0.2757	0.02959	0.458	2.494
Total	4.781	11.56	2.025	18.36	100

Clock Tree Routing

 
- Insertion Delay quite high
 - Try different orientations/ locations



 

Histogram

Not really ideal

 

Critical Path

- Light Blue line
- Start Point: dcache/ from_mem_reg
- End Point: alu_out_MEM_reg



Critical Path (post-syn)

- Clock Period = 1.3 ns
- Slack = 72 ps
- Startpoint:
 - dcache/cpu_offset_reg
- Endpoint:
 - pc_add4_reg

```
Path 1: MET (72 ps) Setup Check with Pin cpu/pc add4 reg[30]/CLK->D
           View: PVT 0P63V 100C.setup view
          Group: clk
     Startpoint: (R) mem/genblk1.dcache/cpu offset reg[1]/CLK
          Clock: (R) clk
       Endpoint: (R) cpu/pc add4 reg[30]/D
          Clock: (R) clk
                     Capture
                                   Launch
                        1300
        Clock Edge:+
                                         0
       Src Latency:+
                                         0
       Net Latency:+
                           0 (I)
           Arrival:=
                        1300
             Setup: -
                         100
       Uncertainty:-
     Required Time:=
                        1193
      Launch Clock: -
         Data Path: -
                        1121
             Slack:=
                          72
```

Critical Path (post-cts)

- Clock Period = 1.3 ns
- Slack = 6.612 ps
- Startpoint
 - dcache/ from_mem_reg
- Endpoint
 - alu_out_MEM_reg

```
Path 1: MET (6.162 ps) Setup Check with Pin cpu/alu out MEM reg[0]/CLK->D
               View: PVT 0P63V 100C.setup view
              Group: reg2reg
         Startpoint: (R) mem/genblk1.dcache/from mem reg/CLK
              Clock: (R) clk
           Endpoint: (R) cpu/alu out MEM reg[0]/D
              Clock: (R) clk
                        Capture
                                       Launch
         Clock Edge:+
                       1300.000
                                        0.000
        Src Latency:+ -250.966
                                     -250.966
        Net Latency:+ 228.900 (P)
                                      272.800 (P)
            Arrival:= 1277.934
                                       21.834
              Setup: -
                          6.339
        Uncertainty:-
                        100.000
        Cppr Adjust:+
                          7.700
      Required Time:= 1179.295
       Launch Clock:= 21.834
          Data Path:+ 1151.299
              Slack:=
                          6.162
     Timing Path:
```

Both post_syn/ post_par are from READ_MEM state in dcache to regs in RISCV core. -> wait for mem_resp_valid & mem_req_ready to generate the STALL signal.

Power Analysis (Switching Power)

Addi.hex	Setup view	Hold view
Static Power (alpha = 0.2)	11.56	17.25
Dynamic Power	1.39	2.29
Activity Factor	2.4%	2.7%

Final.hex	Setup view	Hold view
Static Power (alpha = 0.2)	11.56	17.25
Dynamic Power	1.18	1.94
Activity Factor	2%	2.2%

Summary

- Optimization for frequency
 - 5-stage pipeline
- Optimization for cycles
 - Branch Predictor (2-bit/ 1-bit/ always taken)
 - Write Back Policy
 - Write Buffer in D\$ (Using two FSMs)
- Optimization for area
 - Read-only I\$